

# A Low-Noise Precision Op Amp

National Semiconductor  
Linear Brief 52  
Robert A. Pease  
December 1980



A Low-Noise Precision Op Amp

It is well known that the voltage noise of an operational amplifier can be decreased by increasing the emitter current of the input stage. The signal-to-noise ratio will be improved by the increase of bias, until the base current noise begins to dominate. The optimum is found at:

$$I_{e(\text{optimum})} = \frac{KT}{q} \frac{\sqrt{h_{FE}}}{r_s}$$

where  $r_s$  is the output resistance of the signal source. For example, in the circuit of *Figure 1*, when  $r_s = 1 \text{ k}\Omega$  and  $h_{FE} = 500$ , the  $I_e$  optimum is about  $500 \mu\text{A}$  or  $560 \mu\text{A}$ . However, at this rich current level, the DC base current will cause a significant voltage error in the base resistance, and even after cancellation, the DC drift will be significantly bigger than when  $I_e$  is smaller. In this example,  $I_b = 1 \mu\text{A}$ , so  $I_b \times r_s = 1 \text{ mV}$ . Even if the  $I_b$  and  $r_s$  are well matched at each input, it is not reasonable to expect the  $I_b \times r_s$  to track better than 5 or  $10 \mu\text{V}/^\circ\text{C}$  versus temperature.

A new amplifier, shown in *Figure 2*, operates one transistor pair at a rich current, for low noise, and a second pair at a much leaner current, for low base current. Although this looks like the familiar Darlington connection, capacitors are added so that the noise will be very low, and the DC drift is very good, too. In the example of *Figure 2*, Q2 runs at  $I_e = 500 \mu\text{A}$  and has very low noise. Each half of Q1 is operated at  $11 \mu\text{A} = I_b$ . It will have a low base current (20 nA to 40 nA typical), and the offset current of the com-

posite op amp,  $I_{b1} - I_{b2}$ , will be very small, 1 nA or 2 nA. Thus, errors caused by bias current and offset current drift vs. temperature can be quite small, less than  $0.1 \mu\text{V}/^\circ\text{C}$  at  $r_s = 1000\Omega$ .

The noise of Q1A and Q1B would normally be quite significant, about  $6 \text{ nV}/\sqrt{\text{Hz}}$ , but the  $10 \mu\text{F}$  capacitors completely filter out the noise. At all frequencies above 10 Hz, Q2A and Q2B act as the input transistors, while Q1A and Q1B merely buffer the lowest frequency and DC signals.

For audio frequencies (20 Hz to 20 kHz) the voltage noise of this amplifier is predicted to be  $1.4 \text{ nV}/\sqrt{\text{Hz}}$ , which is quite small compared to the Johnson noise of the  $1 \text{ k}\Omega$  source,  $4.0 \text{ nV}/\sqrt{\text{Hz}}$ . A noise figure of 0.7 dB is thus predicted, and has been measured and confirmed. Note that for best DC balance  $R_6 = 976\Omega$  is added into the feedback path, so that the total impedance seen by the op amp at its negative input is  $1 \text{ k}\Omega$ . But the  $976\Omega$  is heavily bypassed, and the total Johnson noise contributed by the feedback network is below  $1/2 \text{ nV}/\sqrt{\text{Hz}}$ .

To achieve lowest drift, below  $0.1 \mu\text{V}/^\circ\text{C}$ , R1 and R2 should, of course, be chosen to have good tracking tempco, below  $5 \text{ ppm}/^\circ\text{C}$ , and so should R3 and R4. When this is done, the drift referred to input will be well below  $0.5 \mu\text{V}/^\circ\text{C}$ , and this has been confirmed, in the range  $+10^\circ\text{C}$  to  $+50^\circ\text{C}$ . Overall, we have designed a low-noise op amp which can rival the noise of the best audio amplifiers, and at the same

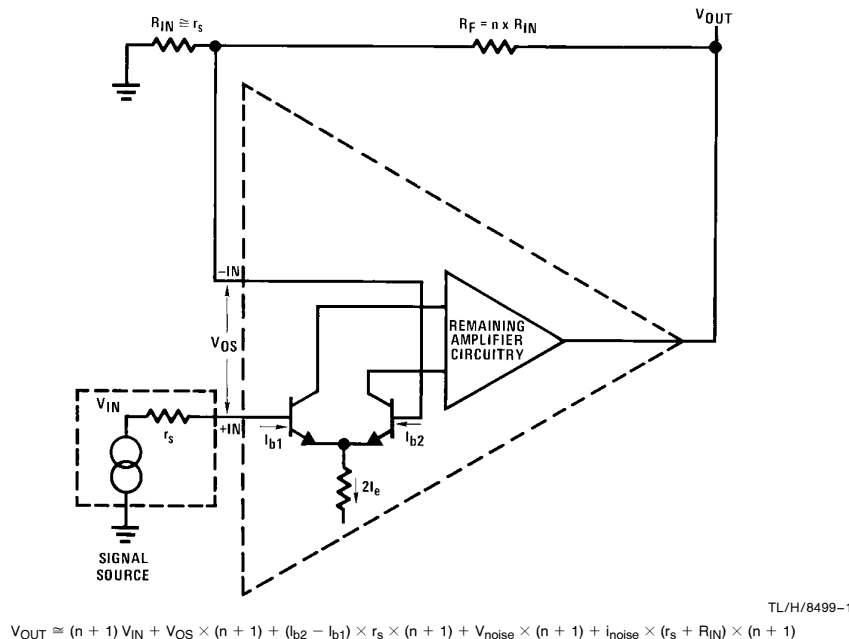


FIGURE 1. Conventional Low-Noise Operational Amplifier

LB-52


To optimize the circuit for other  $r_s$  levels, the emitter current for Q2 should be proportional to  $1/\sqrt{r_s}$ . The emitter current of Q1A should be about ten times the base current of Q2A. The base current of the output op amp should be no more than  $1/1000$  of the emitter current of Q2. The values of R1 and R2 should be the same as R7.

Voltage noise of a transistor, per  $\sqrt{\text{Hz}}$ ,  $e_n = KT \sqrt{\frac{2}{qI_C}}$

Current noise of a transistor, per  $\sqrt{\text{Hz}}$ ,  $i_n = \sqrt{\frac{2qI_C}{h_{FE}}}$

Voltage noise of a resistor, per  $\sqrt{\text{Hz}}$ ,  $e_n = \sqrt{4 KTR_s}$

For a more complete analysis of low-noise amplifiers, see AN-222, "Super Matched Bipolar Transistor Pair Sets New Standards for Drift and Noise", Carl T. Nelson.

 

**FIGURE 2. New Low-Noise Precision Operational Amplifier as Gain-of-1000 Pre-Amp**

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor  
Europe**

Fax: (+49) 0-180-530 85 86  
Email: [cnjwge@tevm2.nsc.com](mailto:cnjwge@tevm2.nsc.com)

Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 52  
Français Tel: (+49) 0-180-532 78 52  
Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor  
Hong Kong Ltd.**  
13th Floor, Straight Block,  
Ocean Centre, 5 Canton Rd.  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor**  
**Japan Ltd.**  
Tel: 81-043-299-2309  
Fax: 81-043-299-2408